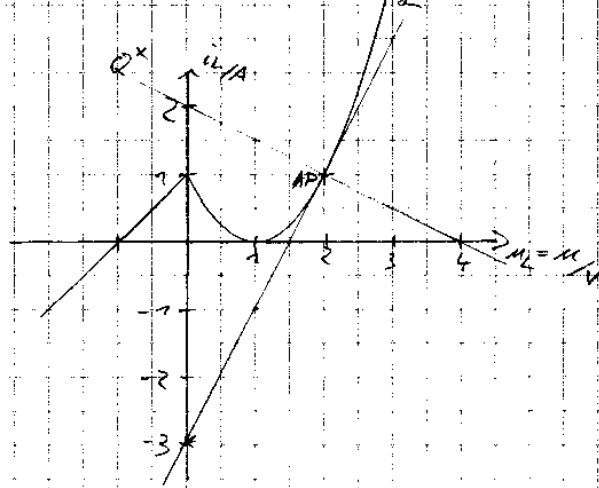


### Aufgabe 5)

a)  $u = R_Q i_Q + u_0$

$$\Rightarrow i_Q = \frac{u}{R_Q} - \frac{u_0}{R_Q} = \frac{1 \text{ A}}{2 \text{ V}} u - 2 \text{ A}$$

b)



c) aktiv, verlustbehaftet, spannungsgesteuert

d)  $i_Q = -i_K$

$$-i_K = \frac{1 \text{ A}}{2 \text{ V}} u - 2 \text{ A}$$

$$i_L = -\frac{1 \text{ A}}{2 \text{ V}} u + 2 \text{ A}$$

e)

$$-\frac{1 \text{ A}}{2 \text{ V}} u + 2 \text{ A} = u^2 \frac{\text{A}}{\text{V}^2} - 2u \frac{\text{A}}{\text{V}} + 1 \text{ A}$$

$$u^2 \frac{\text{A}}{\text{V}^2} - 1,5 \frac{\text{A}}{\text{V}} u - 1 \text{ A} = 0$$

$$u_{1/2} = \frac{1,5 \frac{\text{A}}{\text{V}} \pm \sqrt{2,25 \frac{\text{A}^2}{\text{V}^2} + 4 \frac{\text{A}^2}{\text{V}^2}}}{2 \frac{\text{A}}{\text{V}^2}} = \frac{1,5 \frac{\text{A}}{\text{V}} \pm 2,5 \frac{\text{A}}{\text{V}}}{2 \frac{\text{A}}{\text{V}^2}}$$

$$u_1 = 2 \text{ V} \quad (u_2 = -0,5 \text{ V})$$

$$-\frac{1 \text{ A}}{2 \text{ V}} u + 2 \text{ A} = u \frac{\text{A}}{\text{V}} + 1 \Rightarrow (u = \frac{2}{3} \text{ V})$$


$$\Rightarrow \text{AP}(2 \text{ V}, 1 \text{ A})$$

f)  $i_{L/\text{min}} = \left. \frac{d i_Q}{d u} \right|_{\text{AP}} (u - u_{\text{AP}}) + i_{\text{AP}}$

$$i_{L/\text{min}} = \left( 2u \frac{\text{A}}{\text{V}^2} - 2 \frac{\text{A}}{\text{V}} \right)_{\text{AP}} (u - 2 \text{ V}) + 1 \text{ A}$$

$$i_{L/\text{min}} = 2 \frac{\text{A}}{\text{V}} u - 3 \text{ A}$$

f) (Fortsetzung)

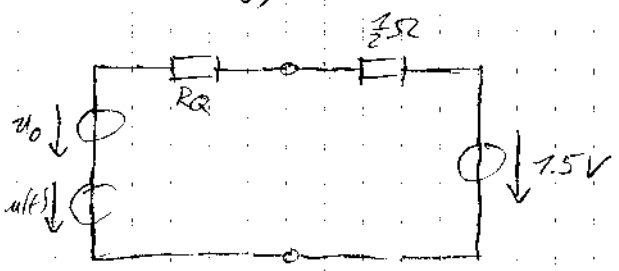

g)

