

Aufgabe 6:

a)  $u_1 = R_1 i_1 + R_3 (i_1 + i_2) = (R_1 + R_3) i_1 + R_3 i_2$   
 $u_2 = R_2 i_2 + R_3 (i_1 + i_2) = R_3 i_1 + (R_3 + R_2) i_2$   $\underline{R} = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_3 + R_2 \end{bmatrix}$

b) passiv, spg-gest., strömgest., reziprok ( $\underline{R} = \underline{R}^T$ )


c)  $\begin{bmatrix} u_1 \\ i_1 \end{bmatrix} = \underline{A} \begin{bmatrix} u_2 \\ -i_2 \end{bmatrix}$

1.  $i_2 = 0$

$$\left. \begin{aligned} u_1 &= R_1 i_1 + R_3 i_1 \\ u_2 &= R_3 i_1 \end{aligned} \right\} \Rightarrow u_1 = \frac{R_1 + R_3}{R_3} u_2$$

$$i_1 = \frac{1}{R_3} u_2$$

2.  $u_2 = 0$

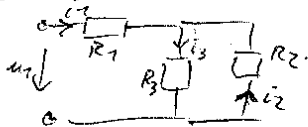

$$u_1 = R_1 i_1 - R_2 i_2$$

$R_2 i_2 + R_3 i_3 = 0$  mit  $i_3 = i_1 + i_2$  folgt

$$(R_2 + R_3) i_2 + R_3 i_1 = 0 \text{ und damit } i_1 = -\frac{R_2 + R_3}{R_3} i_2$$

$$\Rightarrow u_1 = -\frac{R_1}{R_3} (R_2 + R_3) i_2 - R_2 i_2 = -i_2 \left( \frac{R_1 R_2}{R_3} + R_1 + R_2 \right)$$

$$\Rightarrow \underline{A} = \begin{bmatrix} \frac{R_1 + R_3}{R_3} & \frac{R_1 R_2}{R_3} + R_1 + R_2 \\ \frac{1}{R_3} & \frac{R_2 + R_3}{R_3} \end{bmatrix} \begin{bmatrix} u_2 \\ -i_2 \end{bmatrix}$$

mit Umrechnertabelle:

$$\underline{A} = \frac{1}{\det \underline{A}} \begin{bmatrix} + & - \\ - & + \end{bmatrix} \det \underline{A} = \frac{1}{R_3} \begin{bmatrix} R_1 + R_3 & R_1 R_2 + R_1 R_2 + R_3 R_2 \\ -1 & R_2 + R_3 \end{bmatrix}$$


d)  $\pi$ -Glieder

$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \underline{R} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$



$$u_1 = \frac{R_4 R_5}{R_4 + R_5 + R_6} i_1 \quad u_2 = \frac{(R_4 + R_5) R_6}{R_4 + R_5 + R_6} i_1$$

$i_2 = 0$

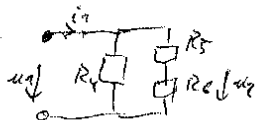


$$u_2 = \frac{R_4 R_6}{R_4 + R_5 + R_6} i_1$$

$$u_1 = \frac{(R_5 + R_6) R_4}{R_4 + R_5 + R_6} i_1$$

$$\Rightarrow \underline{R} = \begin{bmatrix} \frac{(R_5 + R_6) R_4}{R_4 + R_5 + R_6} & \frac{R_6 R_4}{R_4 + R_5 + R_6} \\ \frac{R_4 R_6}{R_4 + R_5 + R_6} & \frac{(R_4 + R_5) R_6}{R_4 + R_5 + R_6} \end{bmatrix}$$

$$e) \begin{aligned} u_1 &= R_1 i_1 + u_{01} + R_3 (i_1 + i_2) + u_{02} \\ u_2 &= R_2 i_2 + R_3 (i_1 + i_2) + u_{02} \end{aligned}$$
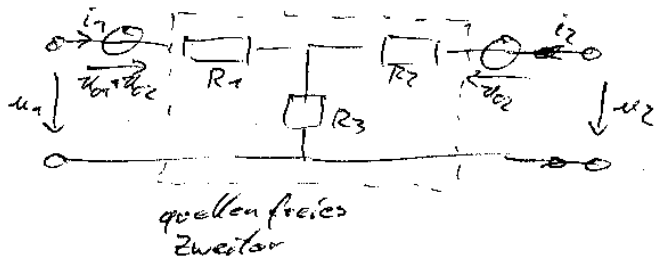
$$\begin{bmatrix} u_1 \\ u_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_3 & R_3 \\ R_3 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix} + \begin{bmatrix} u_{01} + u_{02} \\ u_{02} \end{bmatrix}$$



$$f) \underline{u} = \underline{R} \underline{i} + \begin{bmatrix} u_{01} + u_{02} \\ u_{02} \end{bmatrix}$$

$$\begin{bmatrix} u_1 - u_{01} - u_{02} \\ u_2 - u_{02} \end{bmatrix} = \underline{R} \underline{i} \Rightarrow \begin{bmatrix} 1 & 0 & -R_1 - R_3 & -R_3 \\ 0 & 1 & -R_3 & -R_2 - R_3 \end{bmatrix} \begin{bmatrix} u_1 - u_{01} - u_{02} \\ u_2 - u_{02} \\ i_1 \\ i_2 \end{bmatrix} = \underline{0}$$

$\underbrace{\hspace{10em}}_{-\underline{R}}$

$$g) \left. \begin{aligned} i_1 &= 0A \\ i_2 &= 1A \end{aligned} \right\} \Rightarrow \begin{aligned} u_1 &= 1A R_3 + u_{01} + u_{02} \\ u_2 &= 1A (R_2 + R_3) + u_{02} \end{aligned}$$

$$\left. \begin{aligned} i_1 &= 1A \\ i_2 &= 0A \end{aligned} \right\} \Rightarrow \begin{aligned} u_1 &= (R_1 + R_3) \cdot 1A + u_{01} + u_{02} \\ u_2 &= 1A R_3 + u_{02} \end{aligned}$$

$$\begin{bmatrix} u_1 \\ u_2 \\ i_1 \\ i_2 \end{bmatrix} = \underbrace{\begin{bmatrix} 1A \cdot R_3 & 1A(R_1 + R_3) \\ 1A(R_2 + R_3) & 1A R_3 \\ 0A & 1A \\ 1A & 0A \end{bmatrix}}_{\text{Betriebsmatrix } \underline{B}} \underline{\underline{e}} + \begin{bmatrix} u_{01} + u_{02} \\ u_{02} \\ 0 \\ 0 \end{bmatrix}$$

Betriebsmatrix  $\underline{B}$