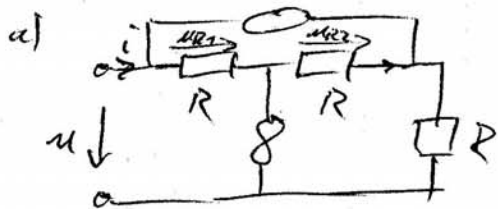



# Aufgabe 5:



$$u_{R1} = Ri \quad u_{R2} = -Ri$$

$$i_{R2} = -i$$

$$\Rightarrow u = -Ri$$

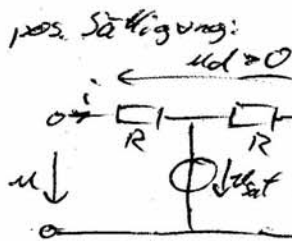


$$u = Ri + u_{sat}$$

$$u_d > 0$$

$$-Ri + \frac{u_{sat}}{2} > 0$$

$$-u + \frac{u_{sat}}{2} > 0$$

$$u < \frac{u_{sat}}{2}$$

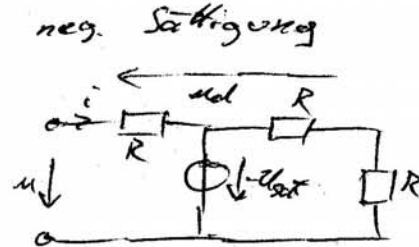


$$u = Ri - u_{sat}$$

$$u_d = -Ri + \frac{u_{sat}}{2} < 0$$

$$-u - \frac{u_{sat}}{2} < 0$$

$$u > \frac{u_{sat}}{2}$$

b)

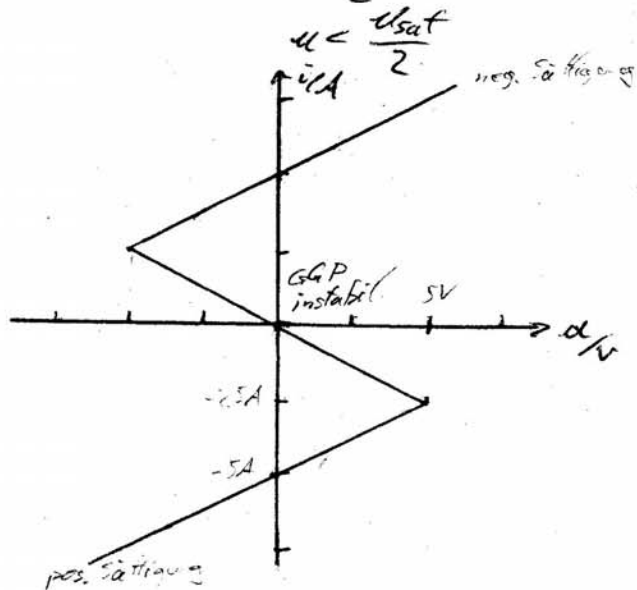

$$\frac{u_{sat}}{R} = \frac{10V}{2.7}$$

$$-i = C\dot{u} \quad i > 0 \Rightarrow u \text{ fällt}$$

$$i < 0 \Rightarrow u \text{ steigt}$$

c)  $u_0 = -Ri_0 = 2.5V$

$$-i = C\dot{u} \Rightarrow C\dot{u} = \frac{u}{R} \Rightarrow \dot{u} = -\frac{u}{RC}$$

$$\Rightarrow u(t) = 2.5V e^{-\frac{t}{RC}} = 2.5V e^{-\frac{t}{25}}$$

$$i = -C \cdot \frac{2.5V}{RC} e^{-\frac{t}{RC}} = -\frac{2.5V}{R} e^{-\frac{t}{RC}} = -7.25A e^{-\frac{t}{25}}$$

$$u(t) = 2.5V e^{-\frac{t}{25}} \stackrel{!}{=} 5V$$

$$t = 25 \ln 2$$

$$-i = C\dot{u} \quad \text{mit } \dot{u} = \frac{u + u_{sat}}{R}$$

$$\Rightarrow \dot{u} = -\frac{u}{RC} + \frac{-u_{sat}}{RC}$$

$$\Rightarrow u(t) = -u_{sat} + [5V + u_{sat}] e^{-\frac{t - 25 \ln 2}{RC}} = -10V + 15V e^{-\frac{t - 25 \ln 2}{RC}}$$

$$i(t) = -C \cdot \frac{15V}{RC} e^{-\frac{t - 25 \ln 2}{RC}} = 7.5A e^{-\frac{t - 25 \ln 2}{RC}}$$

$$u(t) = -10V + 15V e^{-\frac{t - 25 \ln 2}{RC}} \stackrel{!}{=} -5V$$

$$e^{-\frac{t - 25 \ln 2}{RC}} \stackrel{!}{=} \frac{1}{3}$$

$$t - 25 \ln 2 = RC \ln 3$$

$$t = 25 \ln 6$$

$-i = C \dot{u}$  mit  $\dot{u} = \frac{u - u_{sat}}{RC}$

$\Rightarrow \dot{u} = -\frac{u}{RC} + \frac{u_{sat}}{RC}$

$\Rightarrow u(t) = u_{sat} + [-5V - u_{sat}] e^{-\frac{t - 2s \ln 6}{RC}} = 10V - 15V e^{-\frac{t - 2s \ln 6}{RC}}$

$i(t) = -C \frac{(-15V)}{-RC} e^{-\frac{t - 2s \ln 6}{RC}} = -7.5A e^{-\frac{t - 2s \ln 6}{RC}}$


$u(t) = 10V - 15V e^{-\frac{t - 2s \ln 6}{RC}} \stackrel{!}{=} 5V$

$e^{-\frac{t - 2s \ln 6}{RC}} \stackrel{!}{=} \frac{1}{3}$   
 $t - 2s \ln 6 = 2s \ln 3$   
 $t = 2s \ln 18$

Periodendauer  $T_P = 2s \ln 18 - 2s \ln 2 = 2s \ln 9 \approx 4.4s$

$f = \frac{1}{T_P} = \frac{1}{2s \ln 9} \approx 0.23 \text{ Hz}$

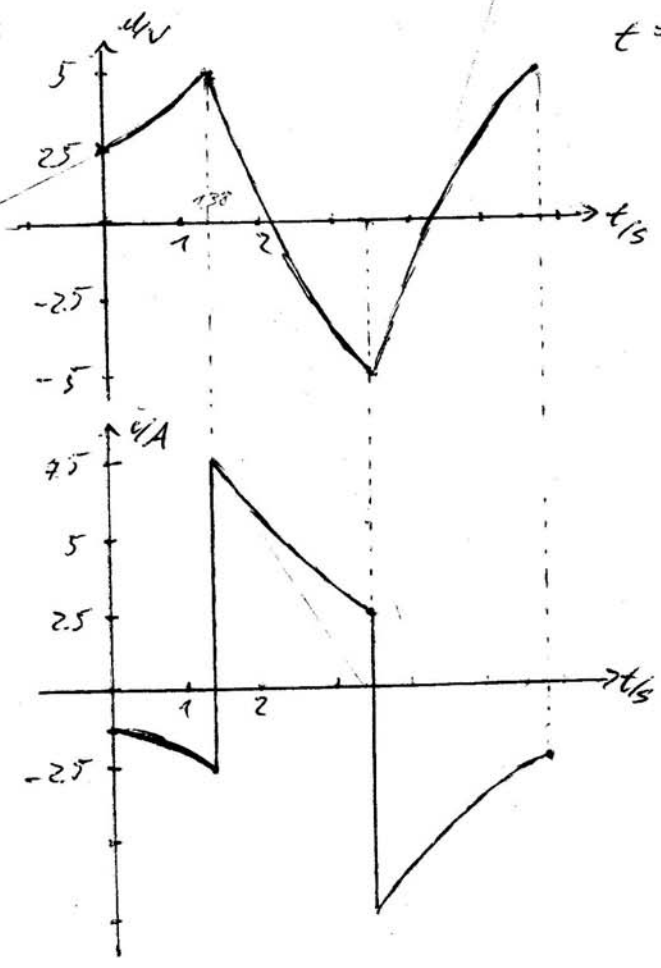Relaxationsoszillator  
 → keine harmonische Schwingung



- d)  $\tau = RC$  ~~muss~~
- Frequenz kleiner → Periodendauer größer
- ⇒  $\tau = RC$  muss steigen
- ⇒ C erhöhen
- ⇒ C parallel  $C_{ges} = C_1 + C_2$

Aufgabe 6:


a)  $u_{C1}, u_{C2}$

b)  $i_{R1} = \frac{u_{in} + u_{C1}}{R_1}$      $i_{R2} = \frac{u_{C2} - u_{C1} - u_{in}}{R_2}$

$i_{R3} = \frac{u_{C2}}{R_3}$

⇒  $i_{C1} = i_{R2} - i_{R1} = \frac{u_{C2}}{R_2} - \frac{u_{C1}}{R_2} - \frac{u_{in}}{R_2} - \frac{u_{in}}{R_1} - \frac{u_{C1}}{R_1}$

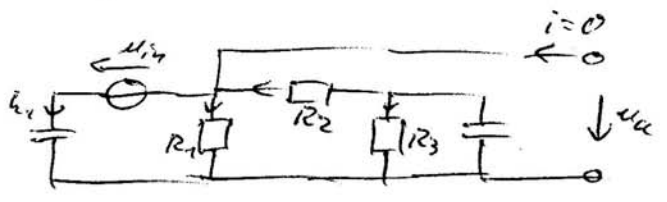$C_1 \dot{u}_{C1} = i_{C1} = u_{C1} \left( -\frac{1}{R_1} - \frac{1}{R_2} \right) + \frac{u_{C2}}{R_2} + u_{in} \left( -\frac{1}{R_1} - \frac{1}{R_2} \right)$   
 $C_2 \dot{u}_{C2} = -i_{R2} - i_{R3} = u_{C2} \left( -\frac{1}{R_2} - \frac{1}{R_3} \right) + \frac{u_{C1}}{R_2} + \frac{u_{in}}{R_2}$



c)  $u_a = R_1 i_{R1} = -\frac{R_1}{R_2} u_{C1} + \frac{R_1}{R_2} u_{C2} - \frac{R_1}{R_2} u_{in} = u_{in} + u_{C1}$   
 Durchgriff  
 Auskopplung (Vektor)  
 Erregung  
 ⇒  $u_a = \begin{bmatrix} \frac{R_1}{R_2} & \frac{R_1}{R_2} \\ -\frac{R_1}{R_2} & \frac{R_1}{R_2} \end{bmatrix} \begin{bmatrix} u_{C1} \\ u_{C2} \end{bmatrix} - \frac{R_1}{R_2} u_{in}$

$\frac{1}{C} \left( \frac{1}{R_1} - \frac{1}{R_2} \right) u_{in}$   
 $\frac{1}{C R_2}$   
 b